

Computer Aided Design CAD

LECTURE 3

Network Equilibrium Equations


□ Loop equations: A branch of a network can, in general, be represented as shown in Fig

where \mathbf{E}_B is the voltage source of the branch.

\mathbf{I}_B is the current source of the branch

\mathbf{Z}_B is the impedance of the branch

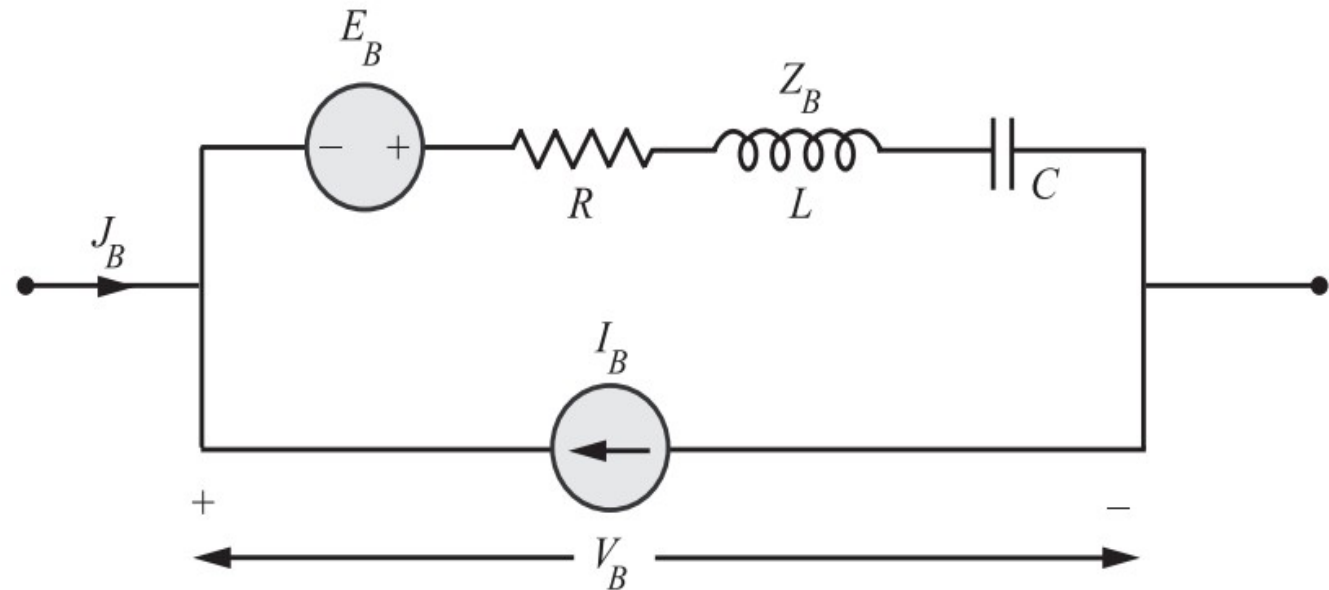\mathbf{J}_B is the current in the branch



Network Equilibrium Equations

The voltage-current relation is then given by

$$\mathbf{V}_B = (\mathbf{J}_B + \mathbf{I}_B) \mathbf{Z}_B - \mathbf{E}_B$$

For a general network with many branches, the matrix equation is

$$\mathbf{V}_B = \mathbf{Z}_B (\mathbf{J}_B + \mathbf{I}_B) - \mathbf{E}_B \quad \Rightarrow \quad \mathbf{V}_B = \mathbf{Z}_B (\mathbf{I}_B + \mathbf{I}_s) - \mathbf{V}_s \quad (1)$$

Where \mathbf{V}_B , \mathbf{J}_B , \mathbf{I}_B , and \mathbf{E}_B are $B \times 1$ vectors and \mathbf{Z}_B is the branch impedance matrix of $B \times B$

Network Equilibrium Equations

Each row of the tie-set matrix corresponds to a loop and involves all the branches of the loop. As per KVL, the sum of the corresponding branch voltages may be equated to zero. That is

$$\mathbf{B}\mathbf{V}_B = \mathbf{0} \quad (2)$$

where \mathbf{B} is the tie-set matrix.

In the same matrix, each column represents a branch current in terms of loop currents. Transposed \mathbf{B} is used to give the relation between branch currents and loop currents.

$$\mathbf{J}_B = \mathbf{B}^T \mathbf{I}_L \quad (3)$$

This equation is called loop transformation equation.

Network Equilibrium Equations

Substituting equation (1) in (2),

$$\mathbf{V}_B = \mathbf{Z}_B (\mathbf{J}_B + \mathbf{I}_B) - \mathbf{E}_B \quad (1)$$

$$\mathbf{B}\mathbf{V}_B = \mathbf{0} \quad (2)$$

we get

$$\mathbf{B}\mathbf{Z}_B \{\mathbf{J}_B + \mathbf{I}_B\} - \mathbf{B}\mathbf{E}_B = \mathbf{0} \quad (4)$$

$$\mathbf{J}_B = \mathbf{B}^T \mathbf{I}_L \quad (3)$$

Substituting equation (3) in (4)

we get

$$\mathbf{B}\mathbf{Z}_B \mathbf{B}^T \mathbf{I}_L + \mathbf{B}\mathbf{Z}_B \mathbf{I}_B - \mathbf{B}\mathbf{E}_B = \mathbf{0}$$

$$\mathbf{B}\mathbf{Z}_B \mathbf{B}^T \mathbf{I}_L = \mathbf{B}\mathbf{E}_B - \mathbf{B}\mathbf{Z}_B \mathbf{I}_B \Rightarrow \mathbf{B}\mathbf{Z}_B \mathbf{B}^T \mathbf{I}_L = \mathbf{B}\mathbf{V}_S - \mathbf{B}\mathbf{Z}_B \mathbf{I}_S$$

Network Equilibrium Equations

Get V_B branch voltage and J_B branch current using cut-set matrix

Each row of the cut-set matrix corresponds to a particular node pair

voltage and indicates different branches connected to a particular node.

KCL can be applied to the node and the algebraic sum of the branch currents at that node is zero.

$$\mathbf{C}\mathbf{J}_B = \mathbf{0} \quad (5)$$

Each column of cut-set matrix relates a branch voltage to node pair voltages.

Hence,

$$\mathbf{V}_B = \mathbf{C}^T \mathbf{E}_N \quad (6)$$

Network Equilibrium Equations

Current voltage relation for a branch is.

$$J_B = Y_B (V_B + E_B) - I_B$$

For a network with many branches the above equation may be written in matrix form as,

$$\mathbf{J}_B = \mathbf{Y}_B \mathbf{V}_B + \mathbf{Y}_B \mathbf{E}_B - \mathbf{I}_B \quad (7)$$

where \mathbf{Y}_B is branch admittance matrix of $B \times B$.

Network Equilibrium Equations

Substituting equation (7) in (5)

$$\mathbf{CJ}_B = 0 \quad (5)$$

$$\mathbf{J}_B = \mathbf{Y}_B \mathbf{V}_B + \mathbf{Y}_B \mathbf{E}_B - \mathbf{I}_B \quad (7)$$

We get

$$\mathbf{CY}_B \mathbf{V}_B + \mathbf{CY}_B \mathbf{E}_B - \mathbf{CI}_B = 0 \quad (8)$$

Substituting equation (6) in (8)

$$\mathbf{V}_B = \mathbf{C}^T \mathbf{E}_N \Rightarrow \mathbf{V}_B = \mathbf{C}^T \mathbf{V}_T \quad (6)$$

We get

$$\mathbf{CY}_B \mathbf{C}^T \mathbf{E}_N = \mathbf{C} (\mathbf{I}_B - \mathbf{Y}_B \mathbf{E}_B) \Rightarrow \mathbf{CY}_B \mathbf{C}^T \mathbf{V}_T = \mathbf{C} \mathbf{I}_S - \mathbf{C} \mathbf{Y}_B \mathbf{V}_S$$

Example

For the network shown in Figure write a tie-set matrix and then find all the branch currents and voltages.

